

## CECS 341 - Lab 4

"ALU Structural Model"

**Due date: 03/01/21**

Student Name: Larry Delgado

Student ID: 016376137

I certify that this submission is my original work



### Lab Report: Lab Assignment X - "Lab title"

1. **Goal:** To learn how to use and setup an ALU in Vivado
2. **Steps:** Followed the procedures for creating a design and test bench module and filled the missing alu op codes.
3. **Results:** The results were 72 cases of various output code
4. **Conclusion:** I learned more about verilog and the challenges were figuring out how some syntax functioned.

### Appendix:

#### Design module:

```
`timescale 1ns/100ps
module alu#(parameter width = 8)
(
    input [width-1:0] a,b,
    input [2:0] aluop,
    output reg [width-1:0] y,
    output reg c,n,z,p
);

always @(a,b,aluop)
```

```

begin
    {y,c,n,z,p} = 0;
    case(aluop)
        0: {c,y} = a + b;
        1: {c,y} = a + 1;
           2: y = a & b;
        3: y = a | b;
           4: y = a ^ b;
        5: y = !a;
        6: {c,y} = a << 1;
        7: y = 0;
        default: y = 32'bZ;
    endcase
    n = y[width-1];
    z = !y;
    p = ^y;
end
endmodule

```

### Output:

[2021-02-22 19:21:16 EST] iverilog '-Wall' design.sv testbench.sv && unbuffer vvp a.out

Test case 0

aluop = 000 a = 1100 b = 0011 y = 1111

c = 0, n = 1, z = 0, p = 0

Test case 1

aluop = 000 a = 0101 b = 1001 y = 1110

c = 0, n = 1, z = 0, p = 1

Test case 2

aluop = 000 a = 1101 b = 0000 y = 1101

c = 0, n = 1, z = 0, p = 1

Test case 3

aluop = 000      a = 1011   b = 1010   y = 0101

c = 1, n = 0, z = 0, p = 0

Test case 4

aluop = 000      a = 1000   b = 1101   y = 0101

c = 1, n = 0, z = 0, p = 0

Test case 5

aluop = 000      a = 0001   b = 0000   y = 0001

c = 0, n = 0, z = 0, p = 1

Test case 6

aluop = 000      a = 1100   b = 1011   y = 0111

c = 1, n = 0, z = 0, p = 1

Test case 7

aluop = 000      a = 0100   b = 0000   y = 0100

c = 0, n = 0, z = 0, p = 1

Test case 8

aluop = 000      a = 1001   b = 1001   y = 0010

c = 1, n = 0, z = 0, p = 1

Test case 9

aluop = 001      a = 1101   b = 0000   y = 1110

c = 0, n = 1, z = 0, p = 1